



Fault Classification of the Error Detection Logic in the Blade Resilient Template

Felipe A. Kuentzer, and Alexandre M. Amory


May 9th, 2016

Pontifícia Universidade Católica do Rio Grande do Sul, Porto Alegre, Brazil



Delay Overheads

 
- Delay margins limits performance gains and increase power consumption





Delay Overheads

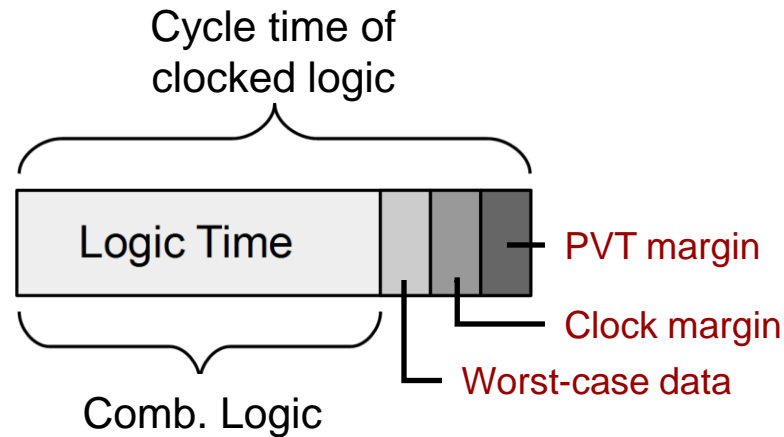
- Delay margins limits performance gains and increase power consumption





Delay Overheads

 - Delay margins limits performance gains and increase power consumption



- Increase desire to operate near threshold voltage levels
 - Challenging in technologies like 45nm, 28nm and below due to PVT

Resilient Design



- Resilient design emerged as a solution to reduce timing margins
- Allow the circuit to operate with relaxed timing constraints
 - Extra logic to detect and recover from timing violations

Resilient Design



- Resilient design emerged as a solution to reduce timing margins
- Allow the circuit to operate with relaxed timing constraints
 - Extra logic to detect and recover from timing violations
- Past synchronous resilient designs
 - Metastability issues
 - High recovery penalties

Resilient Design



- Blade combines the advantages of the asynchronous design and the best features of past resilient schemes
 - 30% power reduction at the same performance for a 10% area overhead

Resilient Design



- Blade combines the advantages of the asynchronous design and the best features of past resilient schemes
 - 30% power reduction at the same performance for a 10% area overhead
- Why resilient designs are not widely used?

Resilient Design



- Blade combines the advantages of the asynchronous design and the best features of past resilient schemes
 - 30% power reduction at the same performance for a 10% area overhead
- Why resilient designs are not widely used?
- Challenges in terms of testability

Testability Issues



- Resilient circuits are inherently tolerant to timing violations
 - Pass/fail criteria needs to be re-examined

Testability Issues



- Resilient circuits are inherently tolerant to timing violations
 - Pass/fail criteria needs to be re-examined
- Area overhead may be critical
 - Limited chip area for test circuitry

Testability Issues



- Resilient circuits are inherently tolerant to timing violations
 - Pass/fail criteria needs to be re-examined
- Limited chip area for test circuitry
 - Area overhead may be critical
- Is functional test enough?
- Can we use existing error detection logic for testing?

Outline




- Blade Template
- Simulation Environment
- EDL Fault Classification
- EDL Fault Analysis
 - Stuck-at Faults
 - Delay Faults
- Conclusions and Next Steps

Blade Template



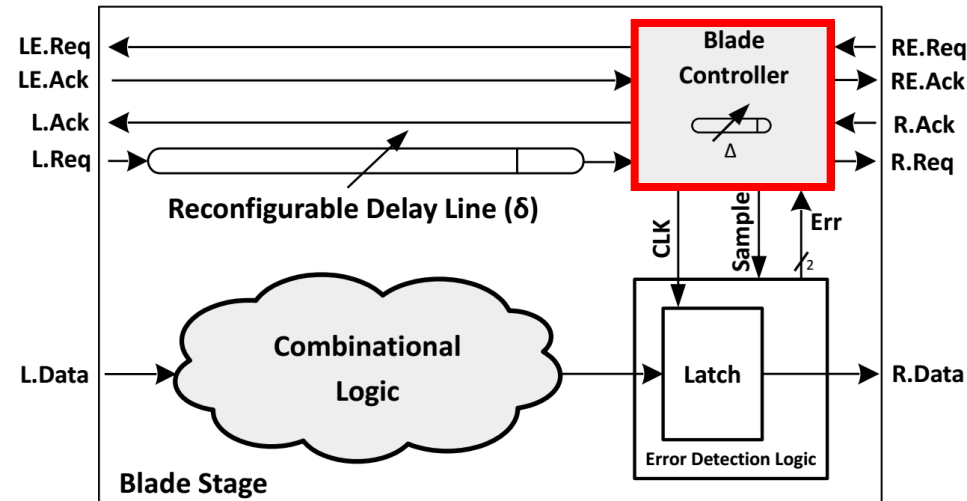- Blade controller
 - Two 2-phase BD channels
 - L and R
 - LE and RE




[Hand et al., ASYNC 2015]

Blade Template



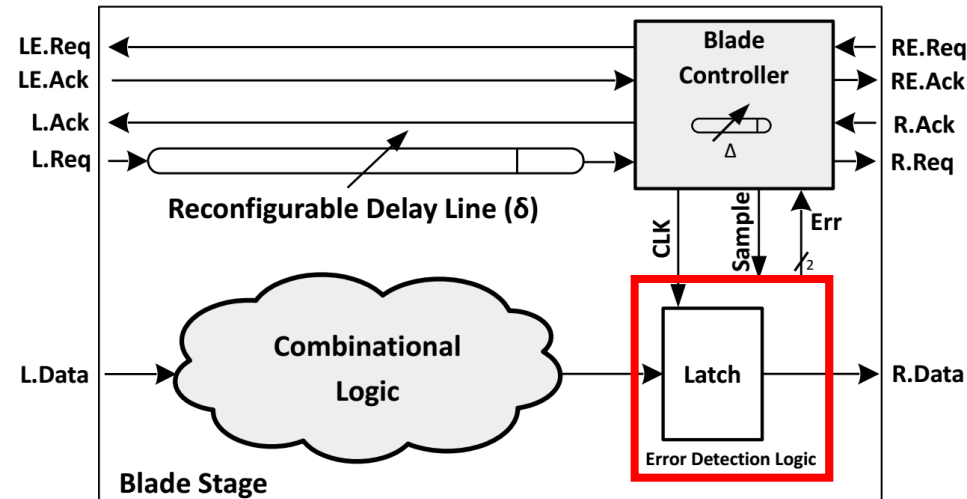- Blade controller
 - Two 2-phase BD channels
 - L and R
 - LE and RE
- Error Detection Logic (EDL)




[Hand et al., ASYNC 2015]




Blade Template

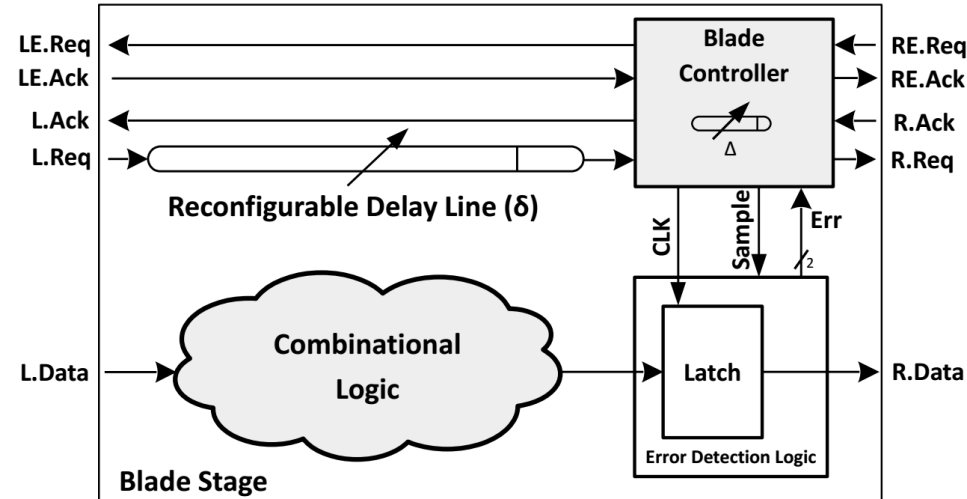- Blade controller
 - Two 2-phase BD channels
 - L and R
 - LE and RE
- Error Detection Logic (EDL)
- Two reconfigurable delay lines
 - δ time where data can be propagate through the EDL
 - Δ time that the latch is transparent




[Hand et al., ASYNC 2015]


Error Detection Logic

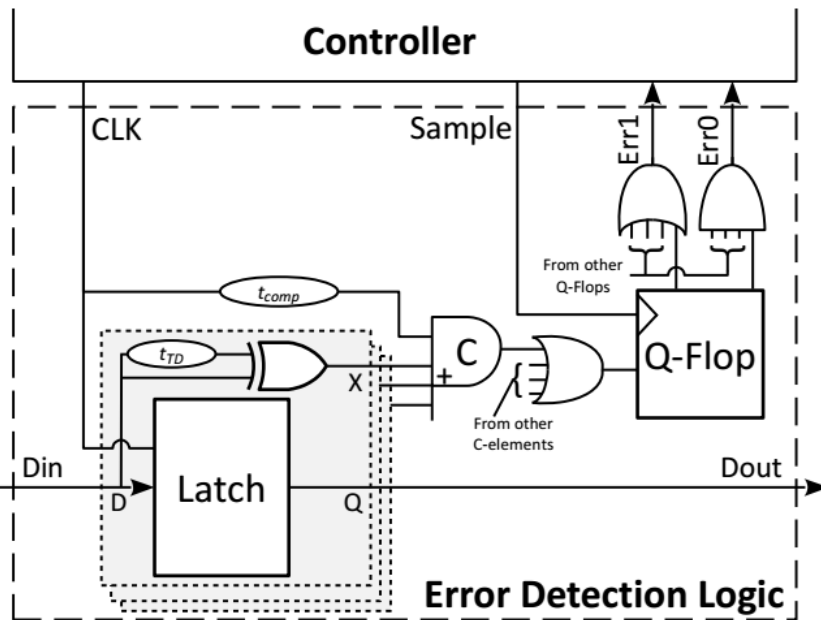


[Hand et al., ASYNC 2015]

 

Error Detection Logic

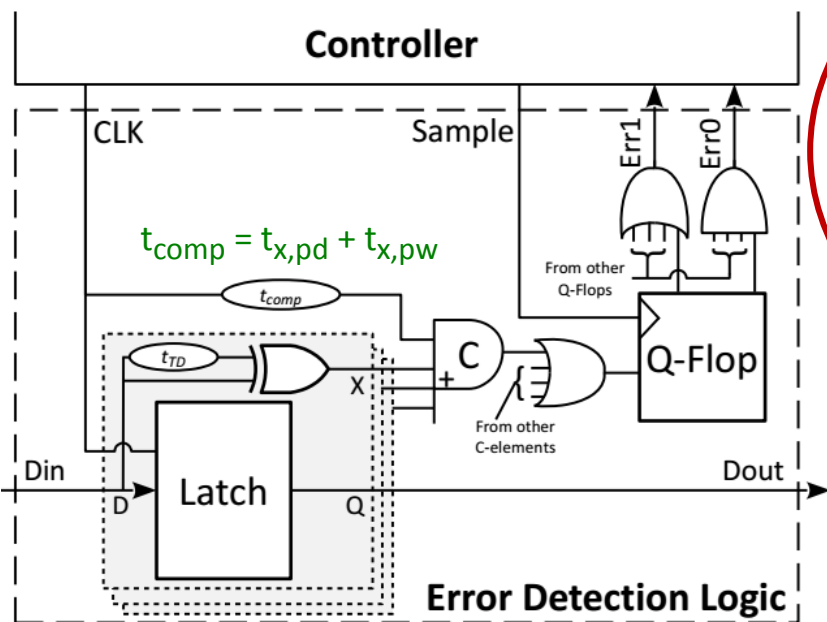


[Hand et al., ASYNC 2015]

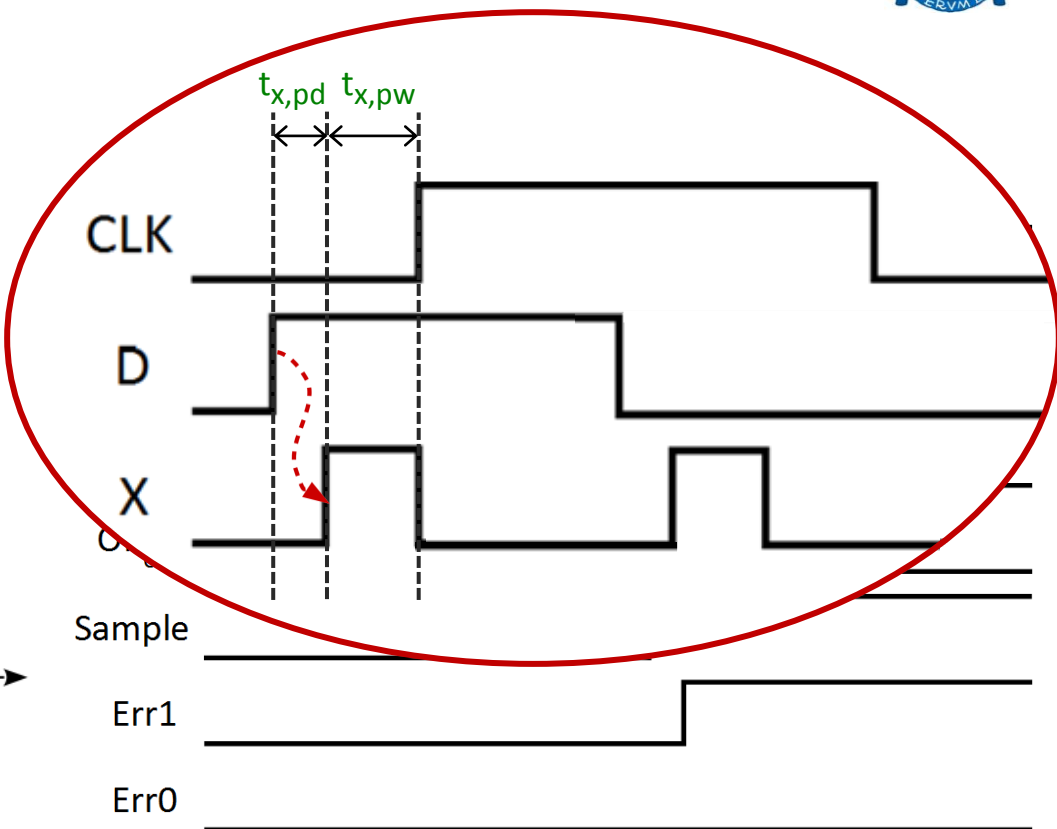





Error Detection Logic

 


[Hand et al., ASYNC 2015]

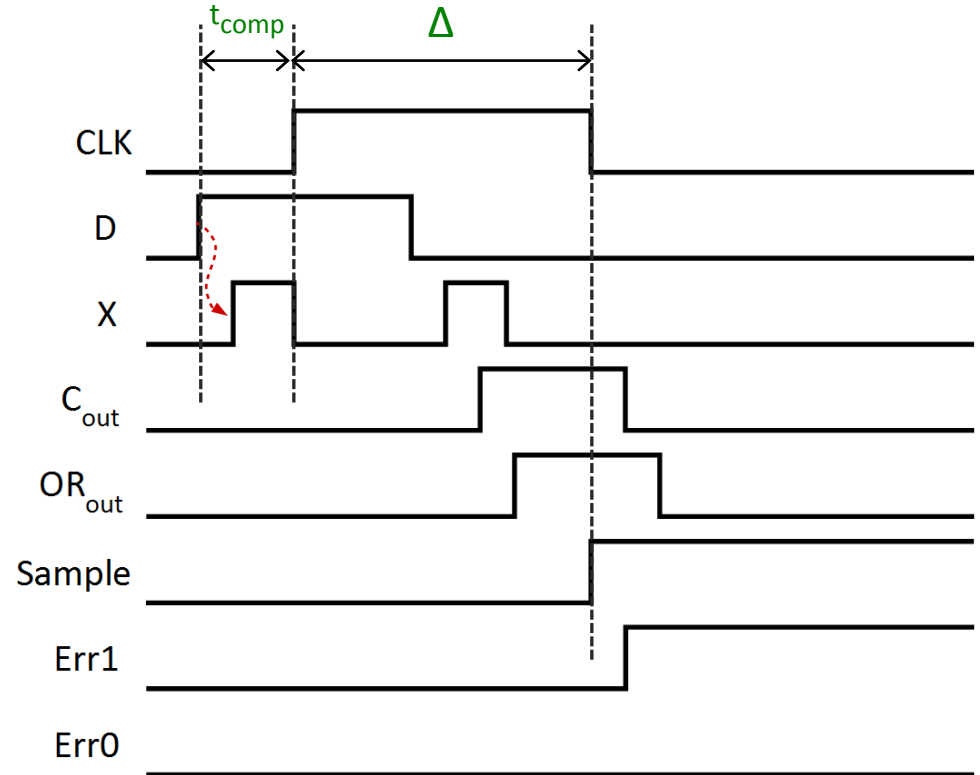

Error Detection Logic

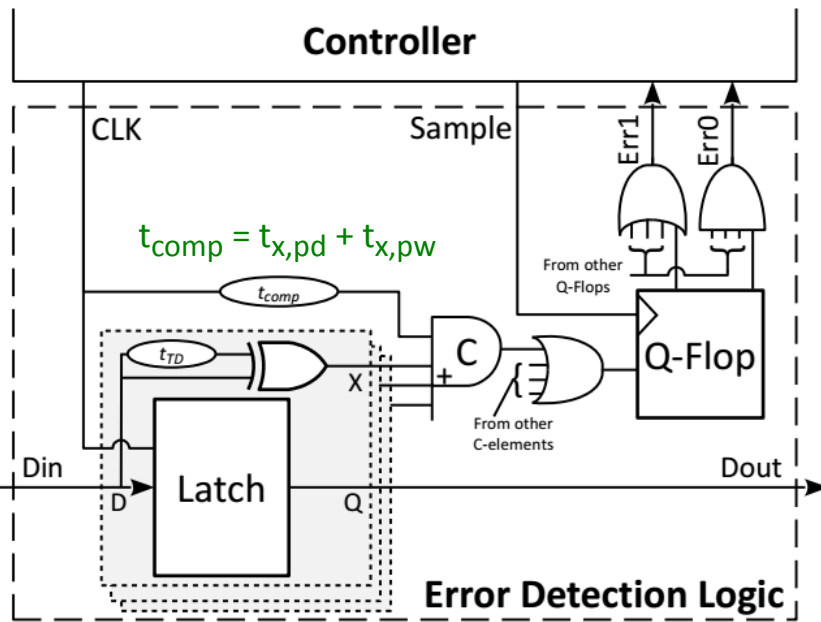


[Hand et al., ASYNC 2015]

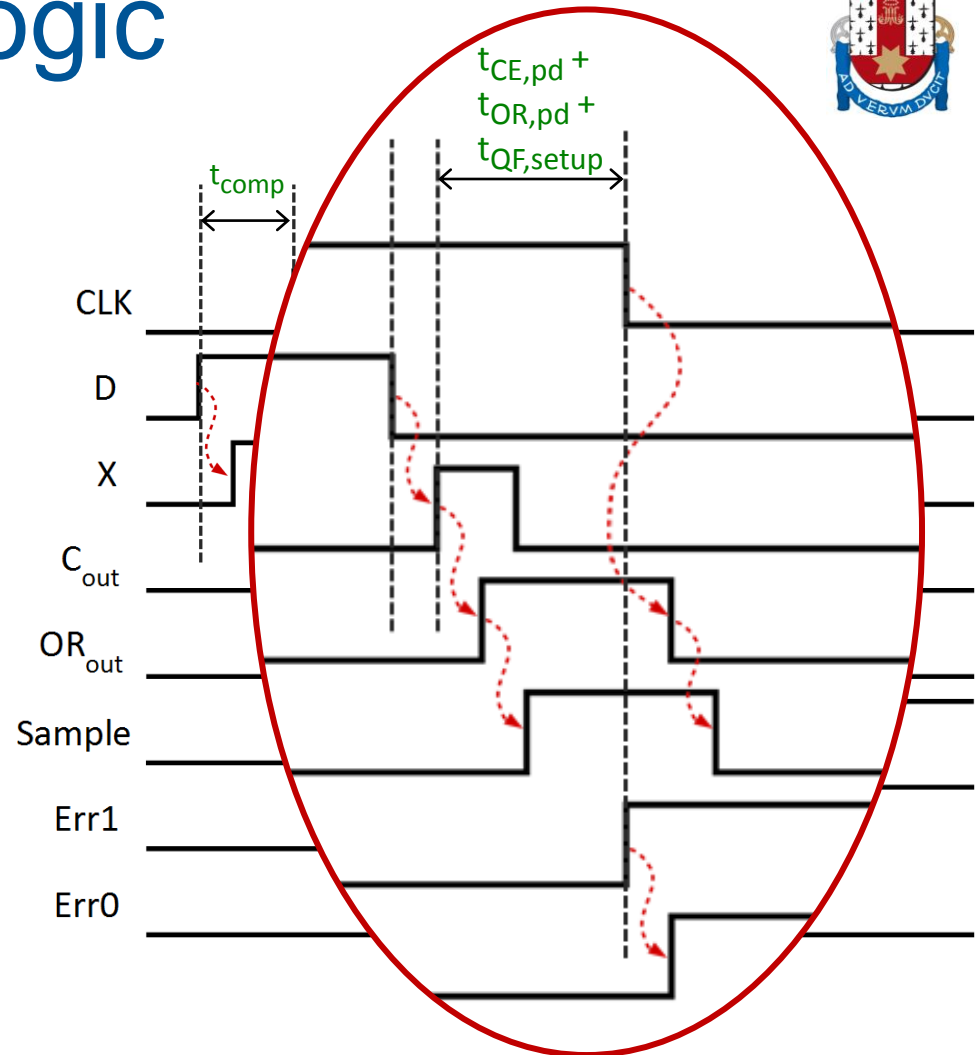




Error Detection Logic

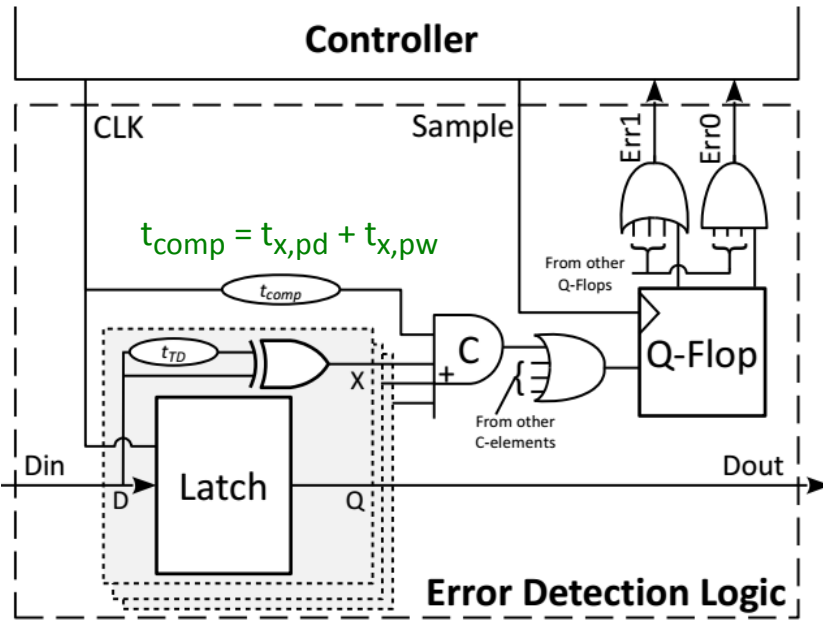

[Hand et al., ASYNC 2015]

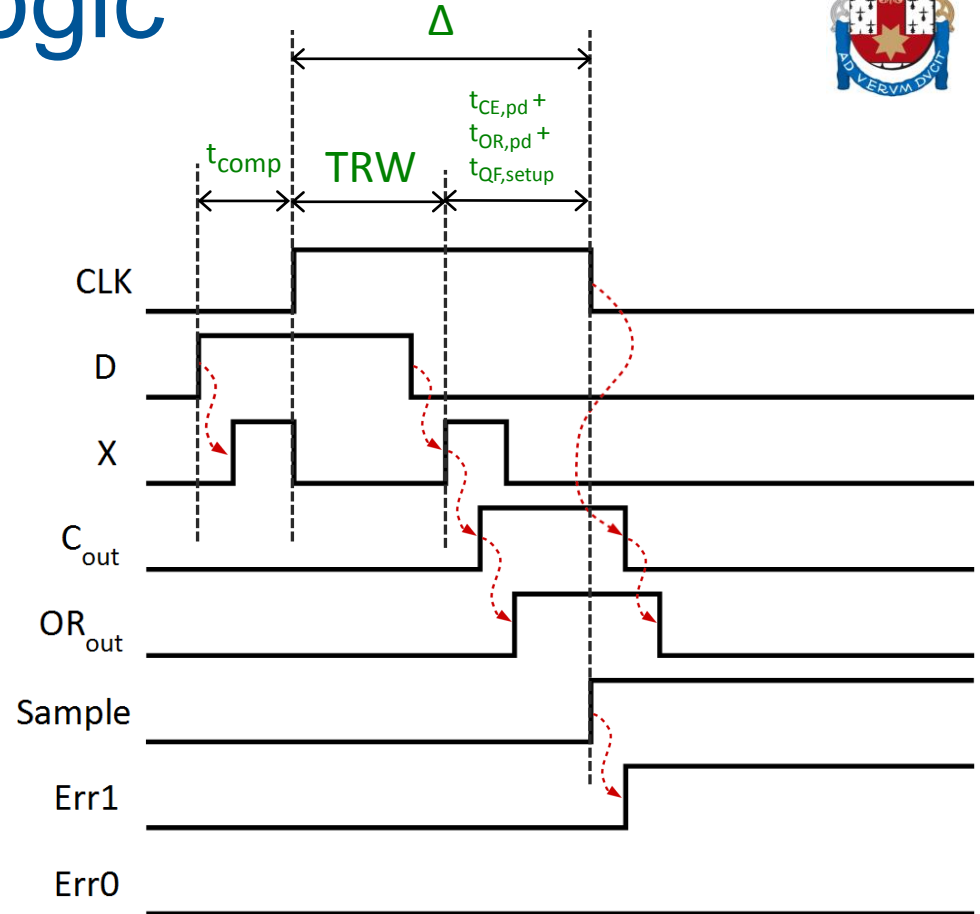

$$TRW = \Delta + t_{X,pw} - (t_{CE,pd} + t_{OR,pd} + t_{QF,setup})$$

Simulation Environment



- Two types of faults are considered
 - Stuck-at faults
 - Wires stuck-at-0 (ST0) stuck-at-1 (ST1)
 - Delay faults
 - Longer propagation delay (LPD)
 - Shorter propagation delay (SPD)

Simulation Environment




- Two types of faults are considered
 - Stuck-at faults
 - Wires stuck-at-0 (ST0) stuck-at-1 (ST1)
 - Delay faults
 - Longer propagation delay (LPD)
 - Shorter propagation delay (SPD)
- Only single faults are considered
- Data is not masked between stages

Simulation Environment




- 3 stage pipeline

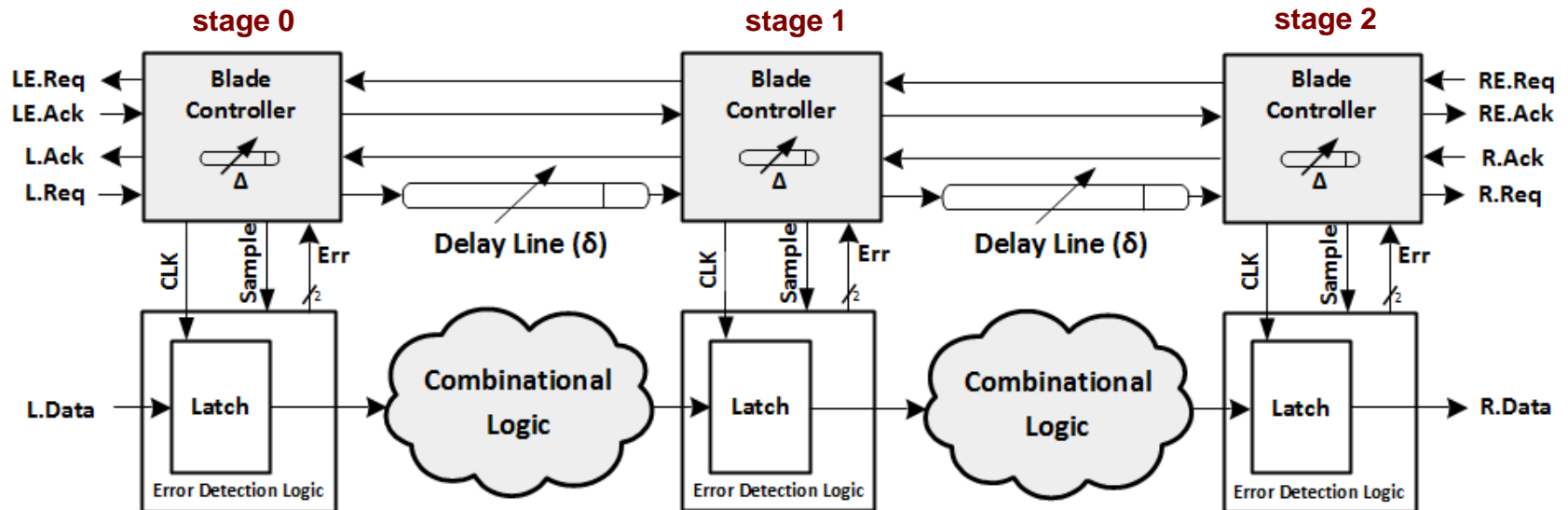

Simulation Environment



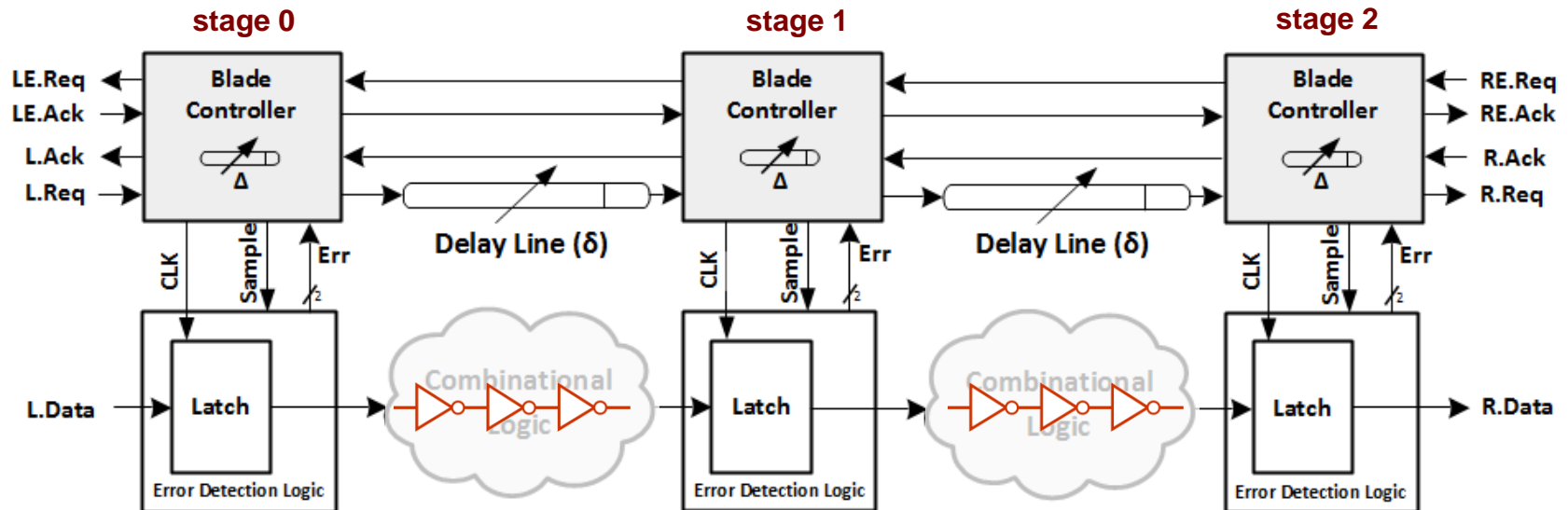
- 3 stage pipeline
 - Dummy combinational logic – balanced stages
 - Timing violations (TV) by extending the inverters delay





Simulation Environment

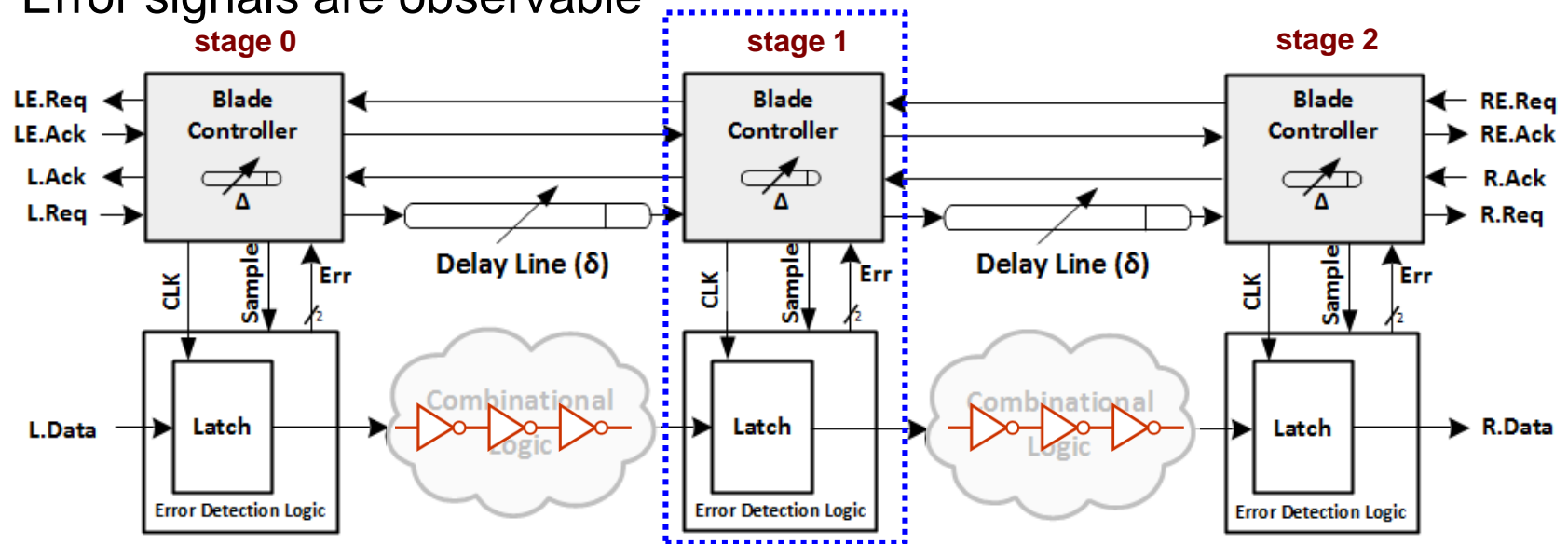- 3 stage pipeline
 - Dummy combinational logic – balanced stages
 - Timing violations (TV) by extending the inverters delay
- Faults are inserted only in stage 1
- Error signals are observable



Fault Classification



- Generalizes the relationship between cause and effect of the analyzed faults

Fault Classification



- Generalizes the relationship between cause and effect of the analyzed faults
- Some faults only affect the performance
- Some faults impact directly the circuit resiliency
 - Disables the EDL



Fault Classification

- Generalizes the relationship between cause and effect of the analyzed faults
- Some faults only affect the performance
- Some faults impact directly the circuit resiliency

– Disables the EDL

UN	undetectable
PST	pipeline output stuck at a value
PH	pipeline halted
ERR_ST	errors in the faulty stage
ERR_NST	errors in the next stage


Fault Classification



UN	undetectable
PST	pipeline output stuck at a value
PH	pipeline halted
ERR_ST	errors in the faulty stage
ERR_NST	errors in the next stage

- Fault classification for stuck-at fault model

Faulty Line	SA0		SA1	
	wo/ TV	w/ TV	wo/ TV	w/ TV
w1	PH	PH	PH	PH
w2	PST	PST	PST	PST
w3	ERR_ST	ERR_ST	ERR_ST	ERR_ST
w4	UN	ERR_NST	ERR_ST	ERR_ST
w5	UN	ERR_NST	ERR_ST	ERR_ST
w6	UN	ERR_NST	ERR_ST	ERR_ST
w7	UN	ERR_NST	ERR_ST	ERR_ST
w8	PH	PH	PH	PH
w9	UN	PH	PH	PH
w10	PH	PH	UN	PH
w11	UN	PH	PH	PH
w12	PH	PH	PH	PH

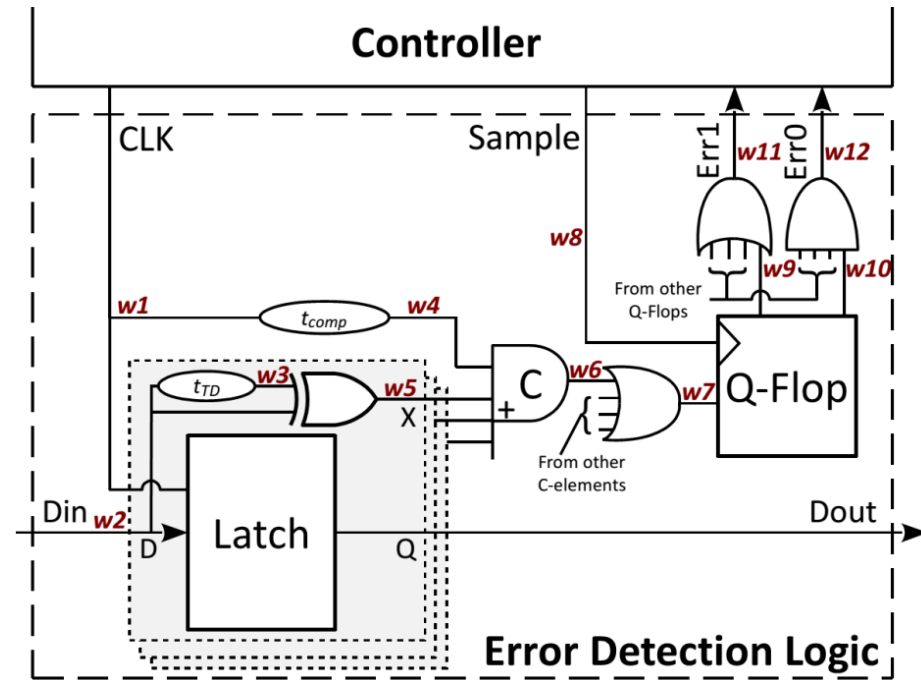


Fault Classification



UN	undetectable
PST	pipeline output stuck at a value
PH	pipeline halted
ERR_ST	errors in the faulty stage
ERR_NST	errors in the next stage

- Fault classification for delay fault model

Faulty Element	SPD		LPD	
	wo/ TV	w/ TV	wo/ TV	w/ TV
Latch	-	-	ERR_NST	ERR_ST / ERR_NST
t_{comp}	ERR_ST	ERR_ST	UN	ERR_ST / ERR_NST
t_{TD}	UN	ERR_NST	ERR_ST	ERR_ST
XOR Gate	-	-	ERR_ST	ERR_ST
C-element	-	-	UN	ERR_NST
OR Gate	-	-	UN	ERR_NST
Q-Flop	-	-	-	-
OR Gate (Err1)	-	-	-	-
AND Gate (Err0)	-	-	-	-

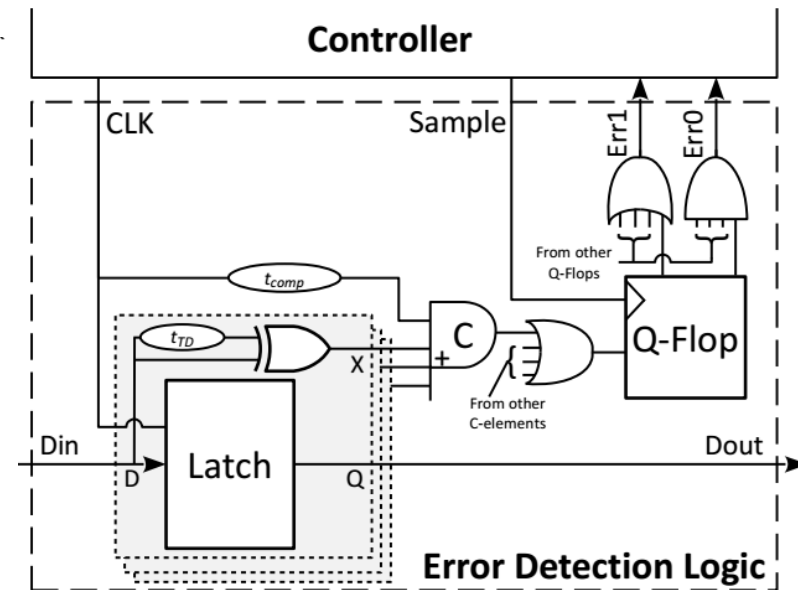


Stuck-at Faults



w1

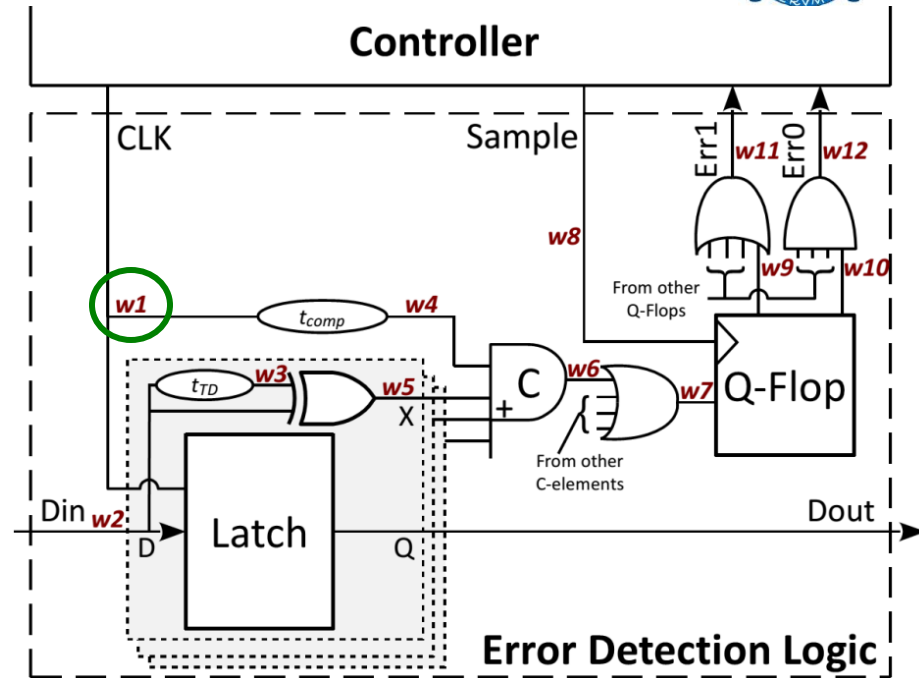- SA0
 - Pipe halts (CLK never rises)
- SA1
 - Pipe halts (CLK never falls)



Stuck-at Faults




w1

- SA0
 - Pipe halts (CLK never rises)
- SA1
 - Pipe halts (CLK never falls)

w4

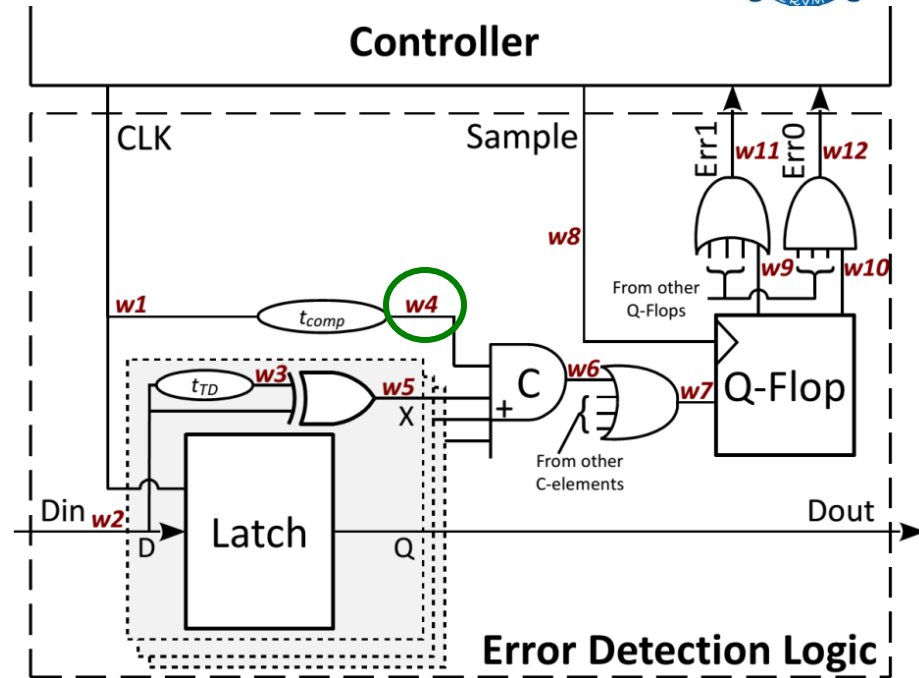
- SA0
 - Error is never captured and TV propagated to the next stage
- SA1
 - Error is always generated, but circuit is still functional



Delay Faults



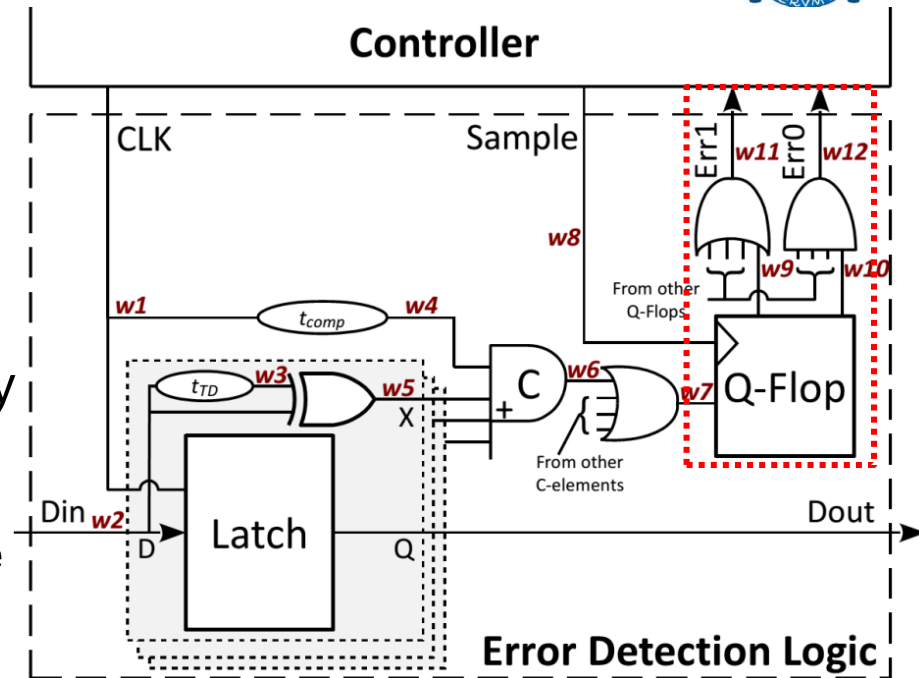
- Q-Flop, OR and AND
 - SPD
 - It won't affect the functionality
 - LPD
 - Only affects the performance



Delay Faults




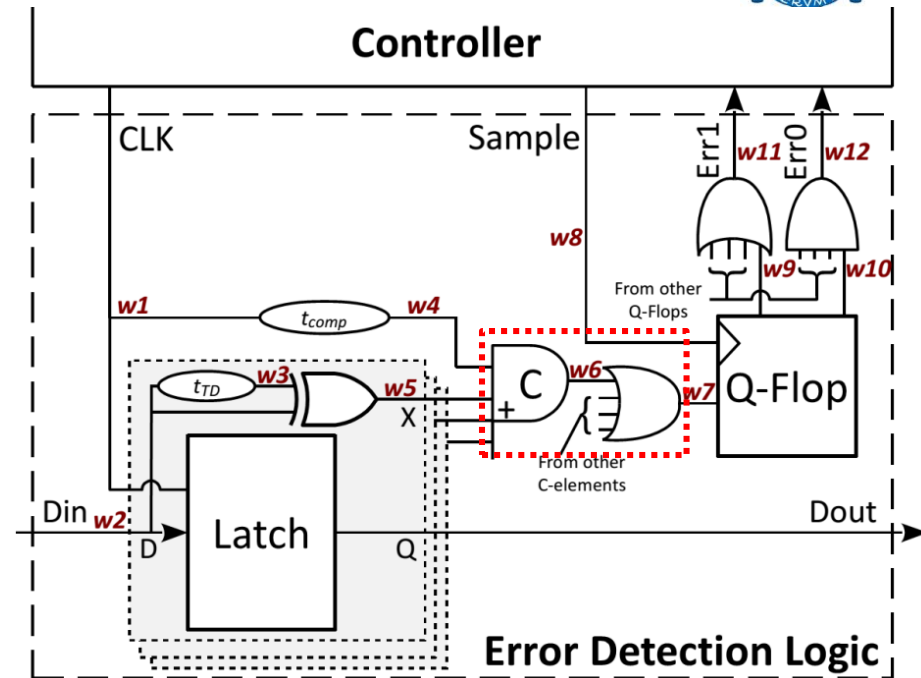
- C-element and OR Gate
 - LPD
 - Can miss a TV





Delay Faults

 
 
- C-element and OR Gate
 - LPD
 - Can miss a TV



Delay Faults



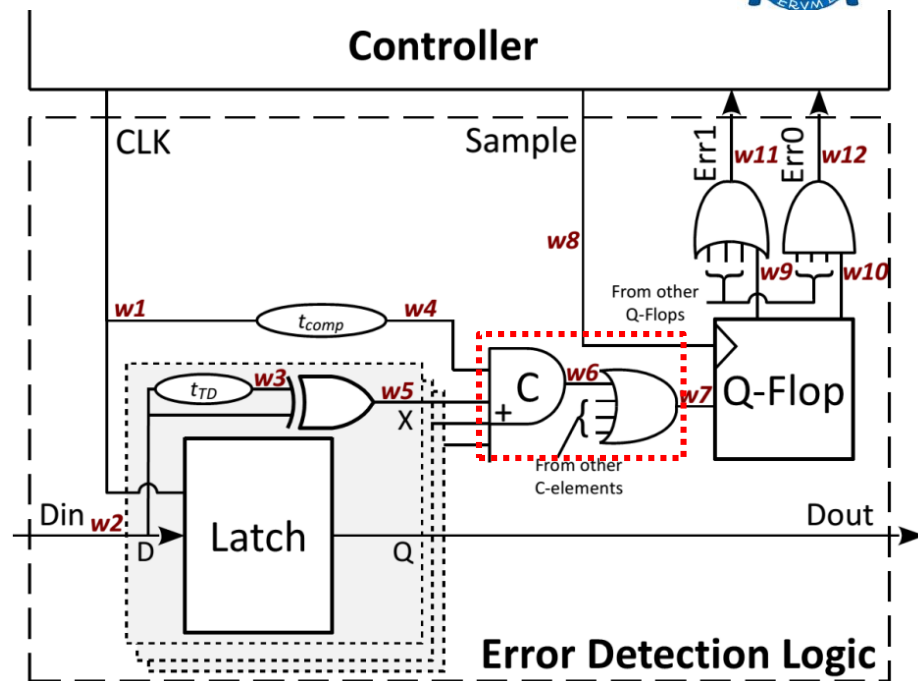
 
- C-element and OR Gate
 - LPD
 - Can miss a TV



Delay Faults



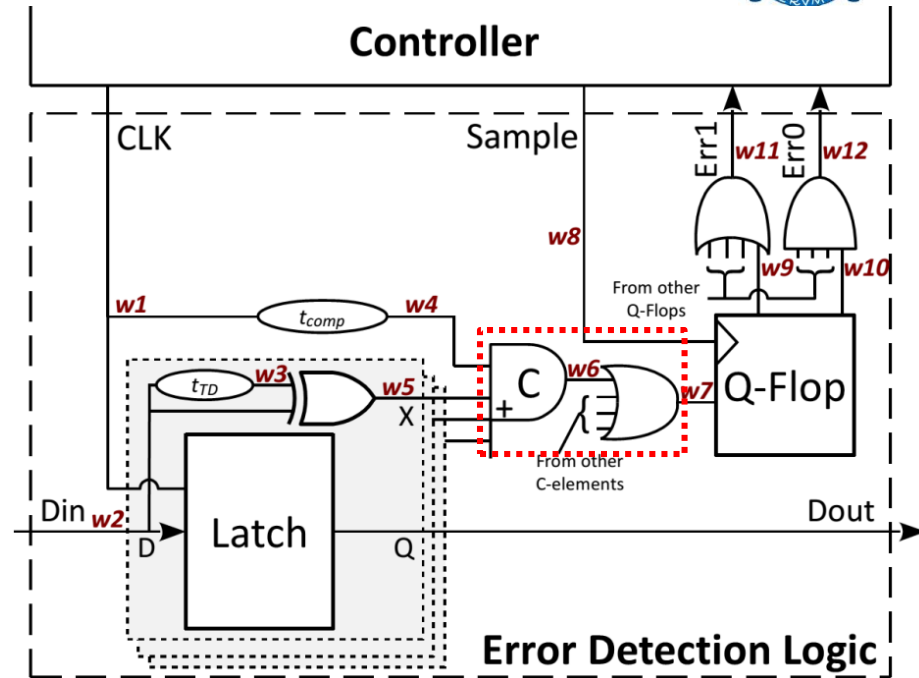
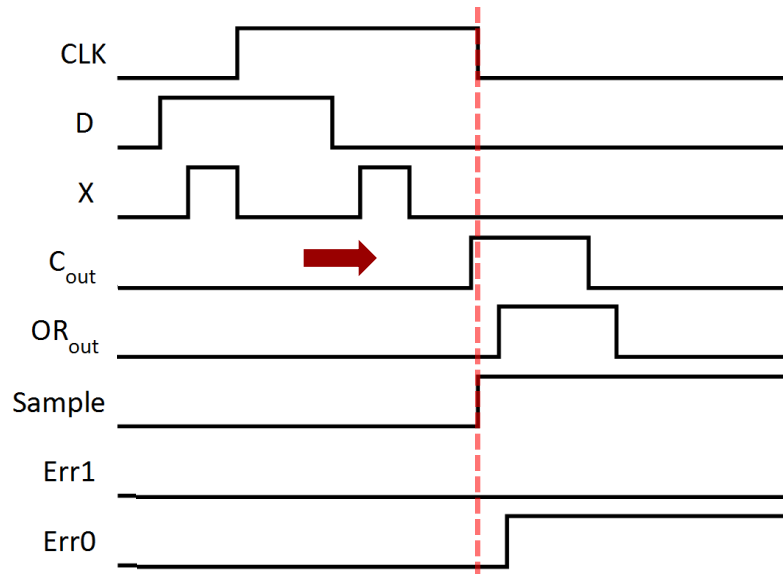
- C-element and OR Gate
 - LPD
 - Can miss a TV



Delay Faults



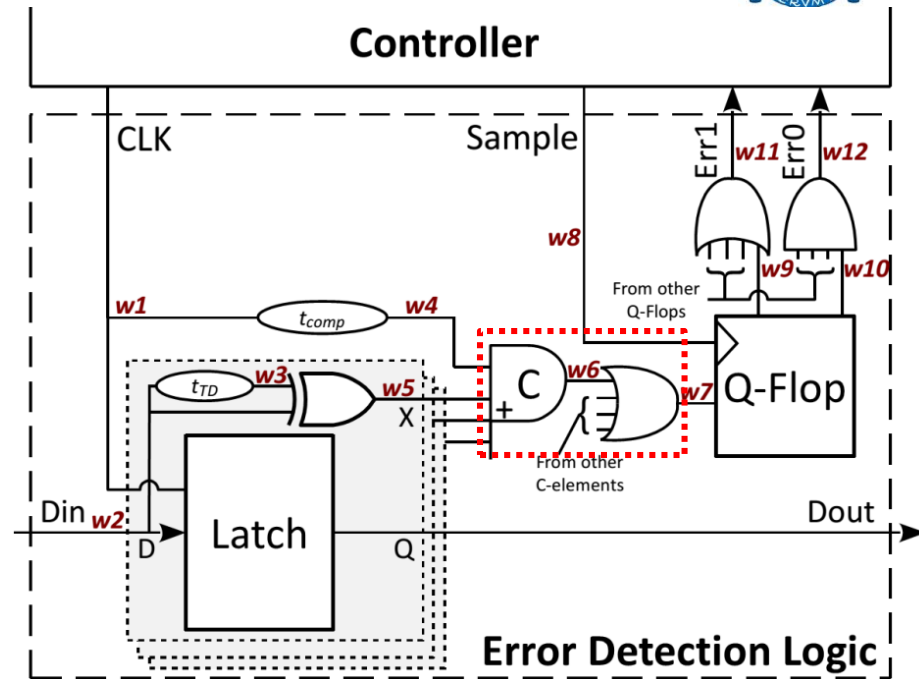 - C-element and OR Gate
 - LPD
 - Can miss a TV
 - Captured by the next state




TV at the end of TRW

Delay Faults




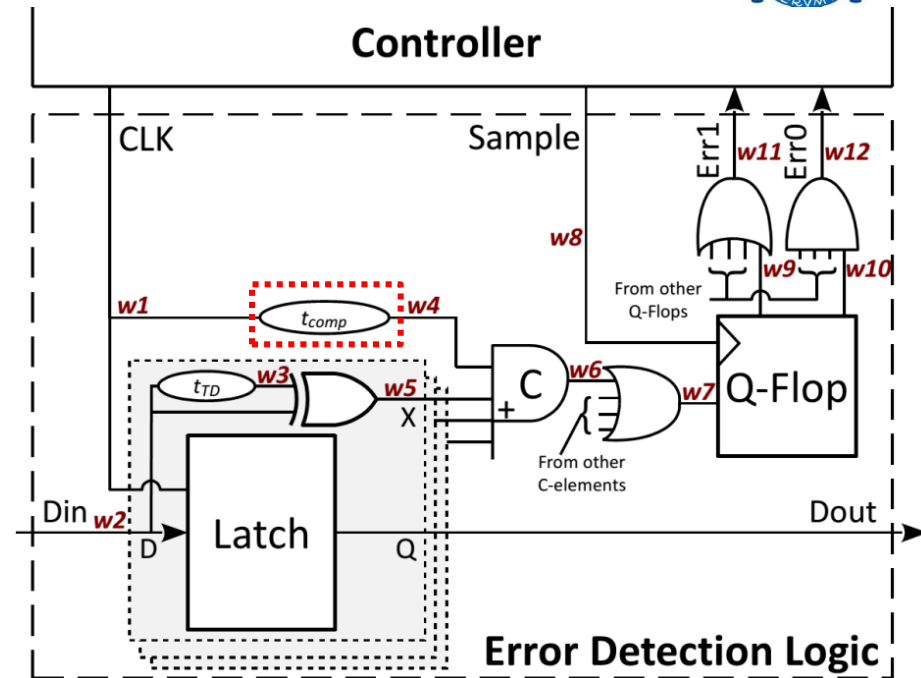
- Delay line – t_{comp}
 - LPD
 - Undetectable without a TV



Delay Faults



 
 
- Delay line – t_{comp}
 - LPD
 - Undetectable without a TV



Delay Faults



 
 
- Delay line – t_{comp}
 - LPD
 - Undetectable without a TV



Delay Faults



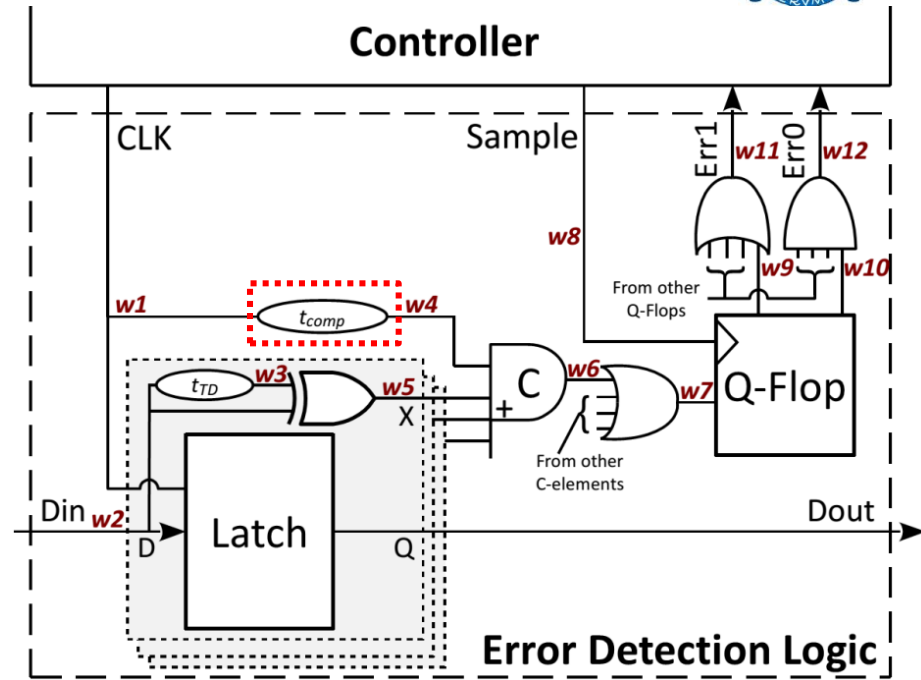
 
- Delay line – t_{comp}
 - LPD
 - Undetectable without a TV





Delay Faults

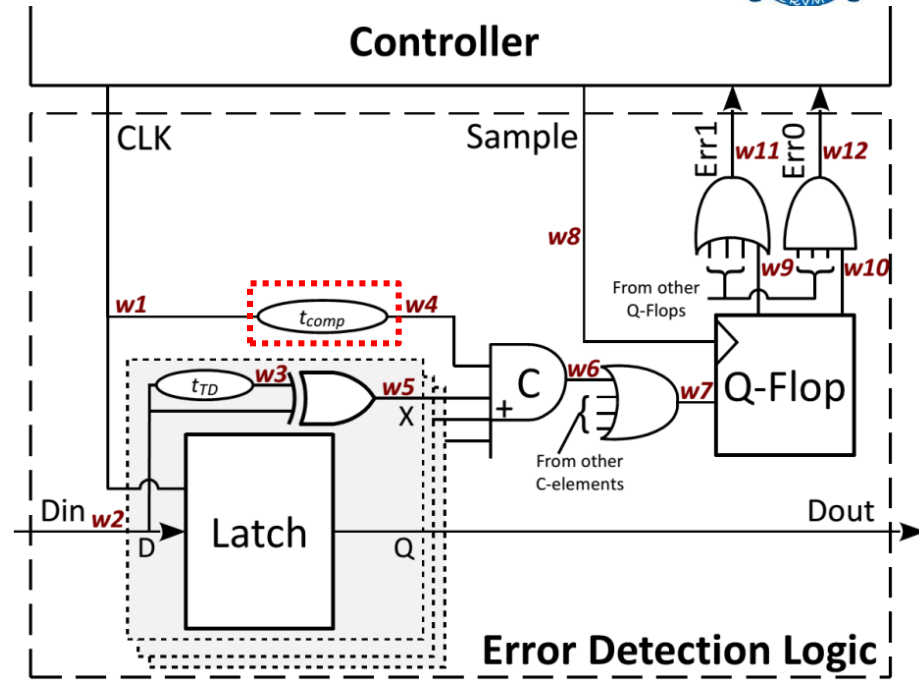
 
- Delay line – t_{comp}
 - LPD
 - Undetectable without a TV



Delay Faults



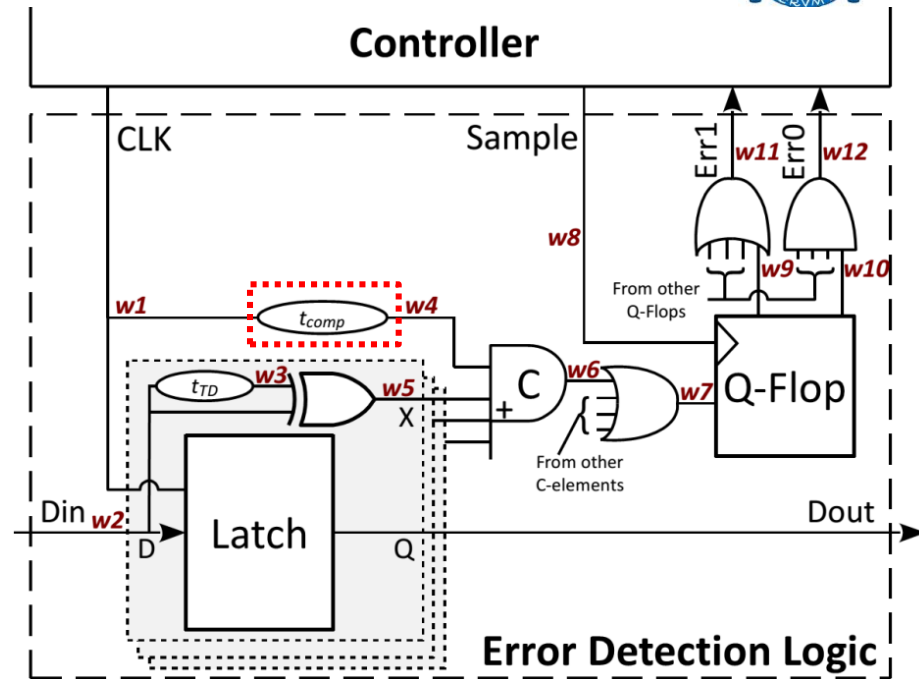
 
- Delay line – t_{comp}
 - LPD
 - Undetectable without a TV



Delay Faults



  - Delay line – t_{comp}
 - LPD
 - Undetectable without a TV
 - TV must be generated



TV at the beginning
of TRW

Test Approaches



- Three approaches evaluated
 - Functional

Test Approaches



- Three approaches evaluated
 - Functional
 - Scan chain
 - Observability of Err1 and Err0



Test Approaches

- Three approaches evaluated
 - Functional
 - Scan chain
 - Observability of Err1 and Err0
 - TV generator
 - Some faults are only observed when the circuit has a TV
 - Glitch generator
 - Delay test pattern

Test Approaches



- Three approaches evaluated
 - Functional
 - Scan chain
 - Observability of Err1 and Err0
 - TV generator
 - Some faults are only observed when the circuit has a TV
 - Glitch generator
 - Delay test pattern

Fault		Functional	Scan Chain	TV Gen.
Type	Wire/ Element			
SA0	w1	*	*	*
	w2	*	*	*
	w3		*	*
	w4			*
	w5			*
	w6			*
	w7			*
	w8	*	*	*
	w9			*
	w10	*	*	*
	w11			*
	w12	*	*	*

Test Approaches



- Three approaches evaluated
 - Functional
 - Scan chain
 - Observability of Err1 and Err0
 - TV generator
 - Some faults are only observed when the circuit has a TV
 - Glitch generator
 - Delay test pattern

Type	Fault		Functional	Scan Chain	TV Gen.
	Wire/ Element				
SA1	w1	*	*	*	*
	w2	*	*	*	*
	w3			*	*
	w4			*	*
	w5			*	*
	w6			*	*
	w7			*	*
	w8		*	*	*
	w9		*	*	*
	w10				*
	w11		*	*	*
	w12		*	*	*

Test Approaches



- Three approaches evaluated
 - Functional
 - Scan chain
 - Observability of Err1 and Err0
 - TV generator
 - Some faults are only observed when the circuit has a TV
 - Glitch generator
 - Delay test pattern

Type	Fault	Functional	Scan Chain	TV Gen.
	Wire/ Element			
SPD	t_{comp}		*	*
	t_{TD}			*
LPD	Latch		*	*
	t_{comp}			*
	t_{TD}		*	*
	XOR Gate		*	*
	C-element			*
	OR Gate			*

Test Approaches

- Three approaches evaluated
 - Functional
 - Scan chain
 - Observability of Err1 and Err0
 - TV generator
 - Some faults are only observed when the circuit has a TV
 - Glitch generator
 - Delay test pattern



Type	Fault	Functional	Scan Chain	TV Gen.
	Wire/Element			
SA0	w1	*	*	*
	w2	*	*	*
	w3		*	*
	w4			*
	w5			*
	w6			*
	w7			*
	w8	*	*	*
	w9			*
	w10	*	*	*
	w11			*
	w12	*	*	*
SA1	w1	*	*	*
	w2	*	*	*
	w3		*	*
	w4		*	*
	w5		*	*
	w6		*	*
	w7		*	*
	w8	*	*	*
	w9	*	*	*
	w10			*
	w11	*	*	*
	w12	*	*	*
SPD	t_{comp}		*	*
	t_{TD}			*
LPD	Latch		*	*
	t_{comp}			*
	t_{TD}		*	*
	XOR Gate		*	*
	C-element			*
	OR Gate			*
Coverage		34%	66%	100%

Test Approaches

- Three approaches evaluated
 - Functional
 - Scan chain
 - Observability of Err1 and Err0
 - TV generator
 - Some faults are only observed when the circuit has a TV
 - Glitch generator
 - Delay test pattern



Type	Fault	Functional	Scan Chain	TV Gen.
	Wire/Element			
SA0	w1	*	*	*
	w2	*	*	*
	w3		*	*
	w4			*
	w5			*
	w6			*
	w7			*
	w8	*	*	*
	w9			*
	w10	*	*	*
	w11			*
	w12	*	*	*
SA1	w1	*	*	*
	w2	*	*	*
	w3		*	*
	w4		*	*
	w5		*	*
	w6		*	*
	w7		*	*
	w8	*	*	*
	w9	*	*	*
	w10			*
	w11	*	*	*
	w12	*	*	*
SPD	t_{comp}		*	*
	t_{TD}			*
LPD	Latch		*	*
	t_{comp}			*
	t_{TD}		*	*
	XOR Gate		*	*
	C-element			*
	OR Gate			*
Coverage		34%	66%	100%

Conclusions and Next Steps



- Fault classification
 - Identify faults based on the effects observed in the overall circuit operation
 - Extract fault coverage for three approaches
 - Design for testability must be incorporated
 - Increase observability and controllability

Conclusions and Next Steps



- Fault classification
 - Identify faults based on the effects observed in the overall circuit operation
 - Extract fault coverage for three approaches
 - Design for testability must be incorporated
 - Increase observability and controllability
- Next steps
 - Investigate alternatives for TV generation
 - Apply this fault analysis and classification to other resilient designs



Questions?

PUCRS



GAPH
Grupo de Apoio ao Projeto de Hardware

Pontifícia Universidade Católica do Rio Grande do Sul