

# Efficient Metastability-Containing Gray Code 2-sort

**Moti Medina**

Joint work with Christoph Lenzen

Max Planck Institute For Informatics, Saarbrücken, Germany



# In The Beginning there was **Metastability**



- Physics

- Analog world (voltage) to 0-1  $\rightarrow$  non 0-1 equilibria = Metastability (Ms).
- [Marino 81] Ms cannot be avoided, detected, or resolved.
- $\uparrow$  clock rate  $\rightarrow$   $\uparrow$  Pr. Metastability.
- $\uparrow$  clock rate  $\rightarrow$   $\uparrow$  #cc until metastability resolves.
- $\uparrow$  #transistors  $\rightarrow$   $\uparrow$  Pr. Metastability.
- **Common solution: Wait!**




- Crossing clock domains
  - Signal arrives out of FF critical segment  $\rightarrow$  Ms.
- **We want to eliminate this reason of Ms.**

# Idea: Clock Synchronization


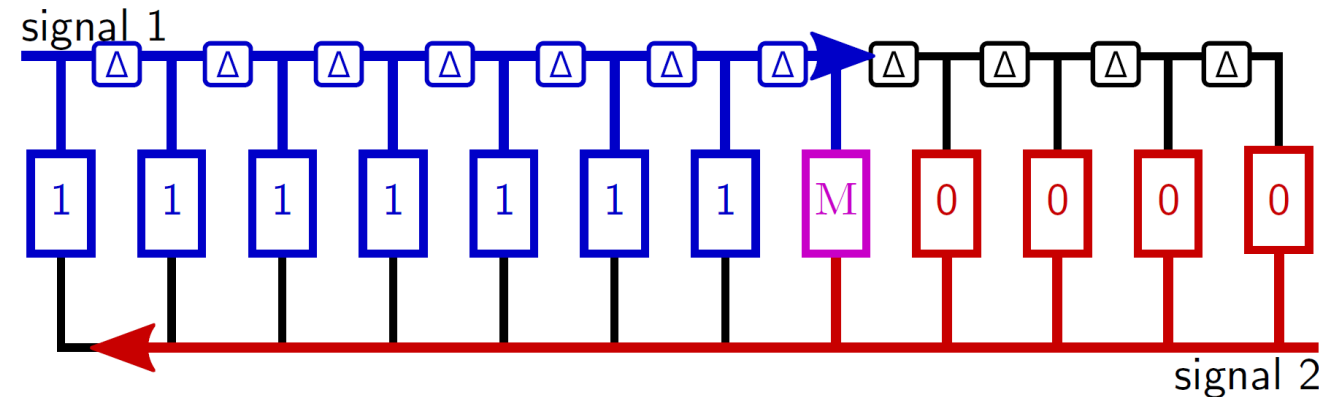
## 1<sup>st</sup> shot: a naïve “solution”

- 2 clocks
- **Master-Slave** approach.
- **Slave** clock measures **Master's** clock.
  - Analog to Digital conversion = a TDC.
- **Slave** clock: Unary to Bin trans and update **slave's** clock.
- Problem: Marino  $\rightarrow$  Metastability.
- Conversion  $\rightarrow$  Arbitrary clock update.
- **Problem: Clock synch. fails.**


  
# 2<sup>nd</sup> shot & Metastability-Containing

- “If you can’t beat them, join them”  
→ **Contain metastability**
- Unary string → analog correction of the oscillator.
  - We didn’t lose any precision due to Ms  
= **metastable containing (Ms-C)**
- Master-slave approach → nice property: bounded phase shift → crossing clock domains doesn’t incur metastability.
- **Problem: the master clock fails → lost availability of a clock, i.e., not a fault tolerant system.**



# Our Goal

- Can we design a system which is
  - fault-tolerant, and
  - No loss of precision due to metastability?
    - i.e., **Containing metastability**






# Yes to Fault-Tolerance!

## The Lynch-Welch [88] Algorithm

- #number of faulty clocks:  $f$
- #number of clocks:  $n = 3f + 1$
- Example:  $f = 2, n = 7$

- Algorithm's idea (animation):

   


### Implementation:

- In each clock (repeat forever)
  - Measure phase diff. from all the other clocks using TDCs.
  - **Sort** these measurements.
  - Adjust self clock to

$$\frac{diff[f+1] + diff[n-f]}{2}.$$
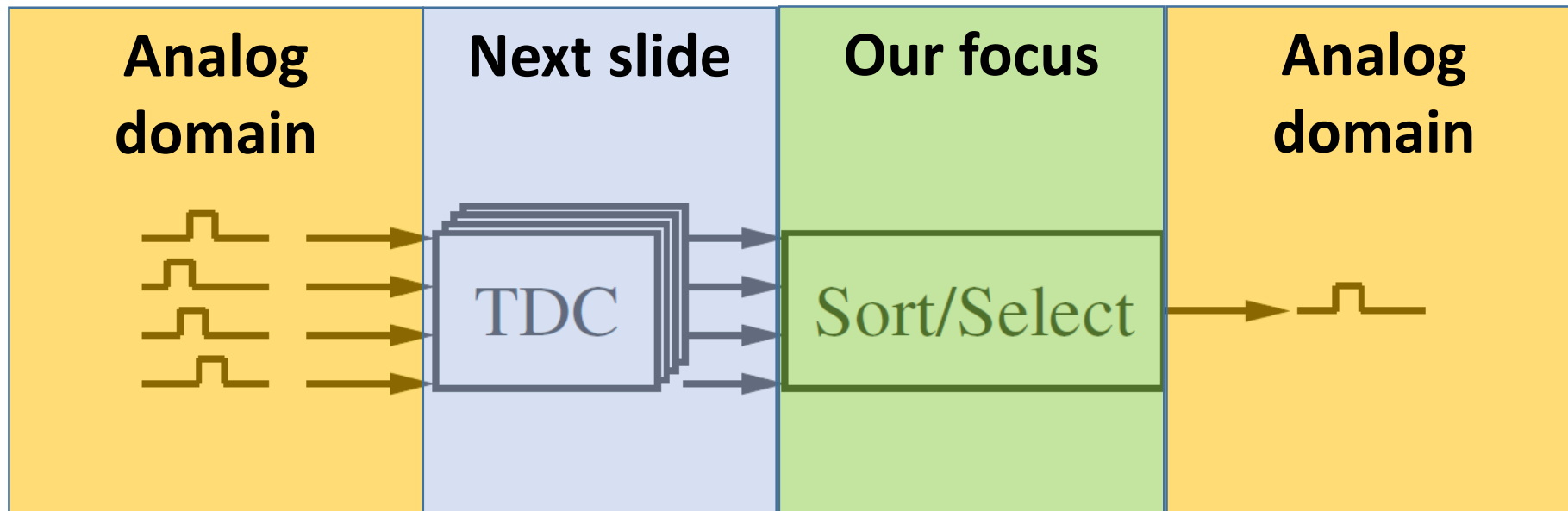
# The System


- Each clock has a  $n - 1$  TDCs.
- Each clock has a [sorting network](#).


 
# Our Time to Digital Converter (TDC)

[Fuegger, Lenzen, Polzer 2016]

- (Ideal) TDC Specification:
  - Input: analog signals  $a(t_1), b(t_2), t_2 > t_1$
  - Output: Gray code representation of  $[t_2 - t_1]$
- Corollary [Marino]: There is no ideal TDC!
- **[FLP2016] : TDC s.t. output contains 1 MS bit,**
  - i.e., in unary  $1^*0^* \cup 1^*M0^*$ ,
  - Mapping to Gray-code in the next slide.
- **Our question revisited: Can we implement the LW algorithm? We cannot wait...**





# Gray code & Valid (input/output) strings

- 3-bit Reflected Binary Gray Code

#	g[1]	g[2]	g[3]
0	0	0	0
1	0	0	1
2	0	1	1
3	0	1	0
4	1	1	0
5	1	1	1
6	1	0	1
7	1	0	0

- Valid (input/output) strings

g[1]	g[2]	g[3]
0	0	M
0	M	1
0	1	M
M	1	0
1	1	M
1	M	1
1	0	M

U

- Valid Unary to Valid Gray code is 1-2-1 & one bit is MS in both.

- $g[1] = M \rightarrow g[2:3]$  is the “biggest” number in two bits Gray code

# Our Question



- We need to sort!
- [LW88] does not solve the **Ms-C** issue.
- Sorting in a **Ms-C** manner + unary strings = exp. size circuits
  - Trivial min/max
  - Who is bigger? 100 or M00 ? 1M0 or 100?



- **Challenge: Find **Ms-C** Polynomial size circuits.**

# Metastability (Ms) model

- Worst case metastability gate propagation.
- Logical masking:

- AND

b \ a	0	1	M
0	0	0	0
1	0	1	M
M	0	M	M

- OR

b \ a	0	1	M
0	0	1	M
1	1	1	1
M	M	1	M

## Cost and Delay of Combinational circ.:

- Standard definitions.
- Cost = sum of basic gates' costs
- Delay = heaviest path from an input to an output.

# Ms-C 2 – *sort* - Specification

- For  $u, v$  unary strings
  - $\max_{un}\{u, v\} = u + v$
  - $\min_{un}\{u, v\} = u \cdot v$
  - $\rightarrow$  **Ms-C**
- For  $u, v$  valid Gray code inputs
  - Let  $\hat{u} \leftarrow un(u), \hat{v} \leftarrow un(v)$
  - $\max_{rg}\{u, v\} = rg\left(\max_{un}\{\hat{u}, \hat{v}\}\right)$
  - $\min_{rg}\{u, v\} = rg\left(\min_{un}\{\hat{u}, \hat{v}\}\right)$
  - $\rightarrow$  **Ms-C**


A MS-C Gray code 2 – *sort*( $B$ ) combinational circuit is defined as follows:

- **Input:**  $B$  bit valid gray code strings  $g, h$
- **Output:**  $B$  bit valid gray code strings  $g', h'$
- **Functionality:**
  - $g' \triangleq \max_{rg}\{g, h\}$
  - $h' \triangleq \min_{rg}\{g, h\}$
 
# Our main result

We propose an **Ms-C** circuit of


- Polynomial cost  $O(B^2)$  , and
- Linear depth  $O(B)$
- that computes the  $2 - \text{sort}(B)$  of two  $B$ -bit Gray code valid inputs.



# Ms-C Multiplexers


- (2: 1)-CMUX

 - Problem: output is Ms even if there is no ``choice''.
- Solution: keep invariant s.t. if  $a = b$  then we ``don't care'' about  $s$




- $(2^k : 1)$ -CMUX

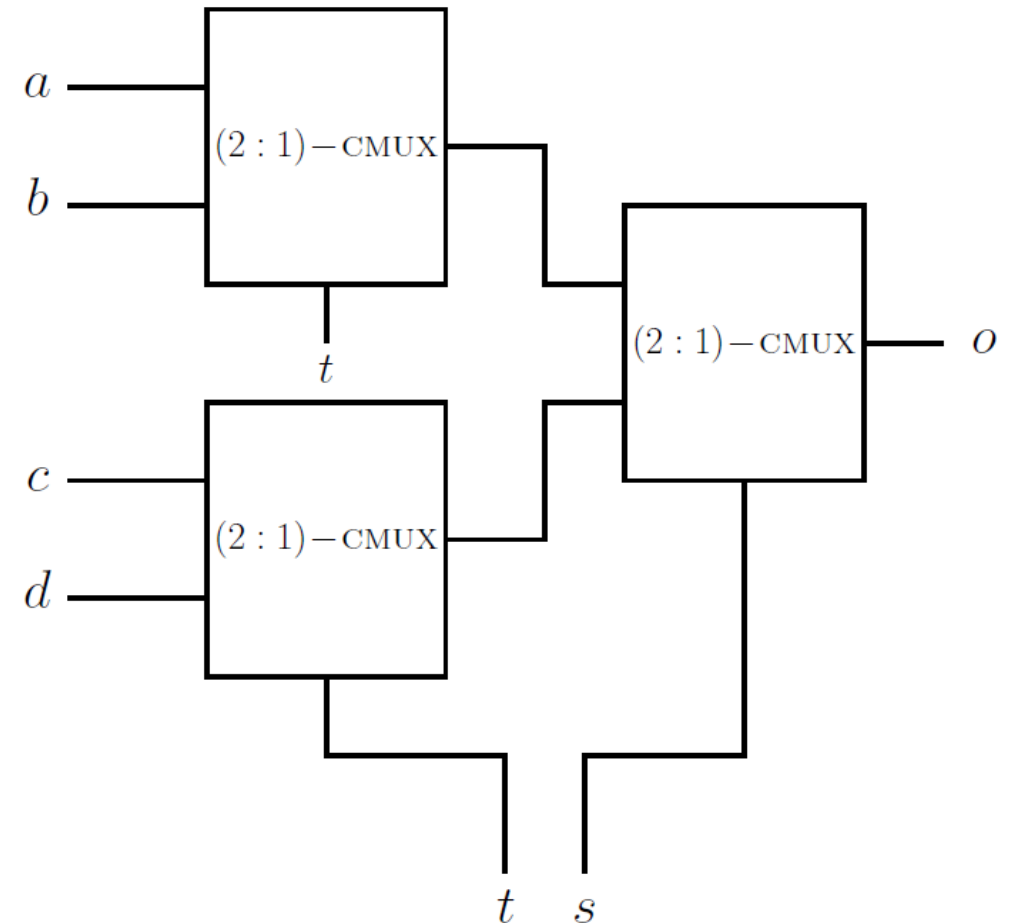- The recursive extension keeps the invariant.


 
## 2 – $sort(B)$ Efficient & Ms-C Design: High Level Idea

- Recursive scheme.
- Directly operates on the Gray code representation.
- Simply branching on the first bit of the code  $\rightarrow$  not Ms-C.




- Observation
  - 1<sup>st</sup> bit Ms  $\rightarrow$  stable bits are the max number.
- Observation + Ms-C Mux
  - both branching options are the same
  - $\rightarrow$  no additional Ms bits!
- Base case:  $B = 1, u, v \in \{0,1\}$ 
  - $\max_{rg}\{u, v\} = u + v$
  - $\min_{rg}\{u, v\} = u \cdot v$

# 2 – $sort(B)$ Design & Proof (by example)

00	$+ = OR$
01	$\cdot = AND$
11	
10	

$g[1]$	$g[2]$
0	0
1	0
1	0

$h[1]$	$h[2]$
1	1
M	1
1	M

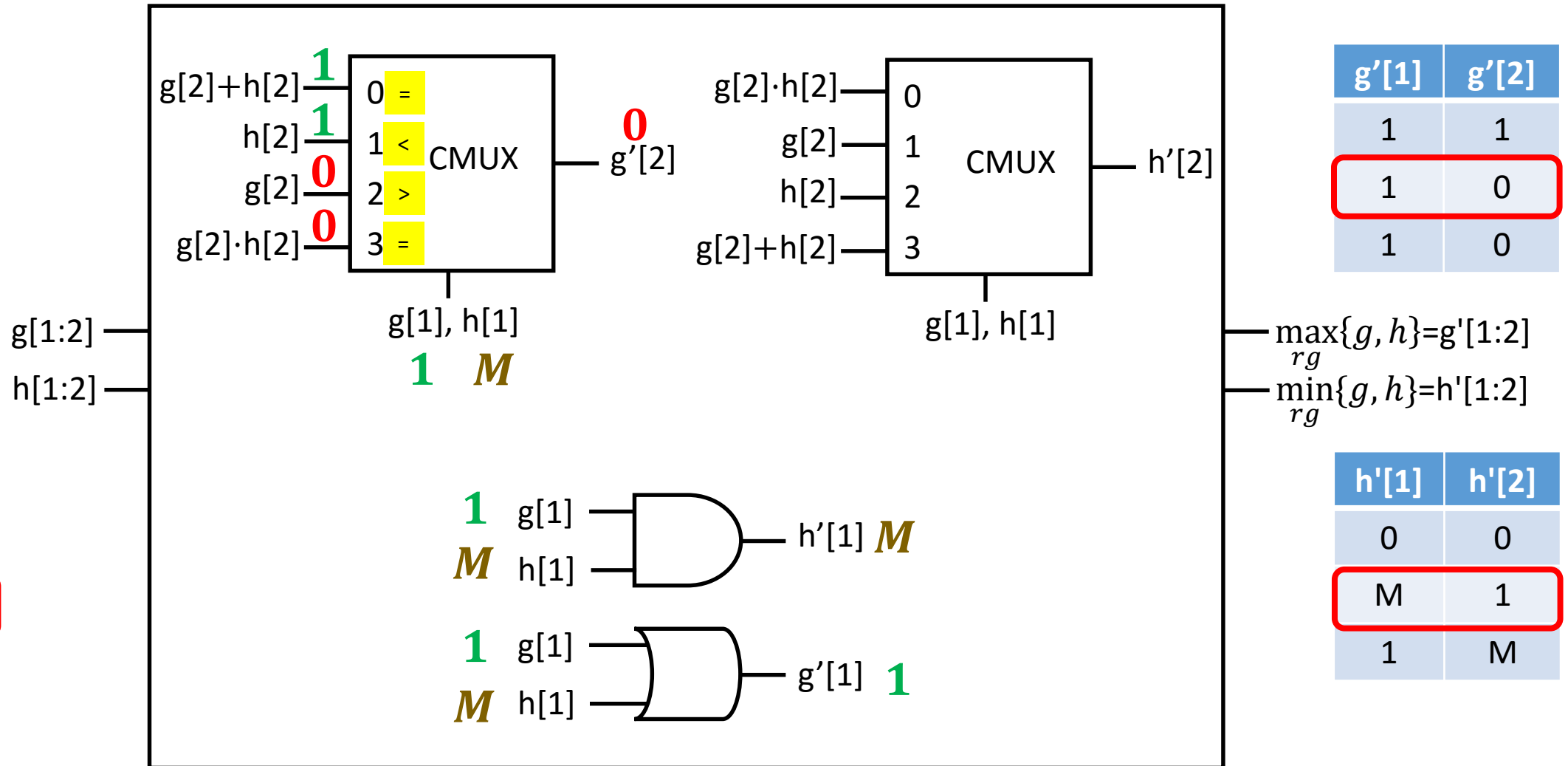


$g'[1]$	$g'[2]$
1	1
1	0
1	0

$h'[1]$	$h'[2]$
0	0
M	1
1	M


 
# Conclusion

- Allowing for computations to take place **before** metastability is resolved.
- Analog measurement **precision is kept**.
- Building an asynchronous system **without synchronizers**.
  - By implementing the LW algorithm




# Further research & Open questions

- More efficient  $2 - \text{sort}(B)$  .



$\log B$  delay  $B \log B$  cost!

 - Design a  $2 - \text{sort}(B)$  that operates on Redundant Binary encoding .
- Super linear delay lower bound for **Ms-C** combinational circuits?
- Replace “Waiting” with **Ms-C** circuits.





*That's all Folks!*