



TECHNISCHE
UNIVERSITÄT
WIEN

Vienna University of Technology

The Metastable Behavior of a Schmitt-Trigger

Andreas Steininger, Jürgen Maier, Robert Najvirt


Embedded Computing Systems
steininger@ecs.tuwien.ac.at

Outline



- What is a Schmitt-Trigger?
- Metastable or not?
- Marino's model
- Analysis of typical scenarios
- The promised answers
- Conclusion & future work

Why a Schmitt-Trigger?

 To turn unclean signals into well-behaved ones appropriate for digital processing





Schmitt-Trigger Operation

  

Hysteresis is attained by making the input threshold depend on current output



Can a Schmitt-Trigger be Metastable?

  - It is “just an inverter with two thresholds”...
- BUT: It must have feedback from the output
- Can this be the perfect RS-latch?



Can this circuit actually work?

  
- *Metastability filter for Muller C-element*
- Where is the gain if the Schmitt-Trigger gets metastable itself?



Does this circuit work safely?


- A *clock-handshake interface*
- Integrators produce monotonic waveform
- “The outputs of the integrators have been augmented with Schmitt-trigger inverters to guarantee quick transitions...”

⇒ What about S/T metastability?

 

What about input filtering?

 
- *Huffman's Inertial Delay Element*
- Low pass at S/T input to prevent metastability
- Perfect ID allows building a perfect synchronizer
- Can this ID implementation be perfect?



- This is analyzed in Marino's paper



Marino's Model

 - Based on ideal op-amp with positive feedback
- First order low pass to limit output dynamics





Marino's Model

  - Phase plane shows (meta-) stable state
- Equations for derivative of output w.r.t. time





Realistic Implementations

  - We used realistic op-amp models in HSPICE simulations
 - Commercial op-amp model (EL5165)
 - CMOS implementation (With 65 nm library)





Model vs. Simulation

  - They differ in quantitative details but give the same qualitative results





Strictly Monotonic Inputs

  



Once tripped, trajectory cannot move back
to a metastable state $\Rightarrow$ clean transitions

Monotonic Input Trace Staying Constant

  

Can stay indefinitely long on tripping point, *i.e.* metastable with clear HI at output $\Rightarrow$ late transition

Producing Intermediate Output

  


With an appropriate input, the S/T can be made metastable

➡ “constant” output depending on input; resolving to HI/LO




Not what we know from latch et al.

Producing Arbitrary Output

 


Moving input while S/T resolves moves metastable voltage
 ➡ arbitrary waveforms while metastable

Perfect Latch Revisited

 


There is no perfect latch!

 


The other circuits



 Works safely – monotonic
input once C-element resolves



Not safe!


 


Safe but late
transitions possible

Conclusions

- S/T may become metastable
- Output voltage may have any value when metastable
- strictly monotonic input $\Rightarrow$ clean transition
- constant input at tripping point $\Rightarrow$ late transition
- non-monotonic input $\Rightarrow$ any waveform possible

Future Work: S/T Cascade

  

Needs three dimensions for the characteristic

Conclusions

- S/T may become metastable
- Output voltage may have any value when metastable
- Strictly monotonic input $\Rightarrow$ clean transition
- Constant input at tripping point $\Rightarrow$ late transition
- Non-monotonic input $\Rightarrow$ any waveform possible

Thank you!