


EXERCÍCIOS SOBRE CIRCUITOS DE CHAVES

Fonte: J. Daghljan. Lógica e Algebra de Boole.


i)



ii)

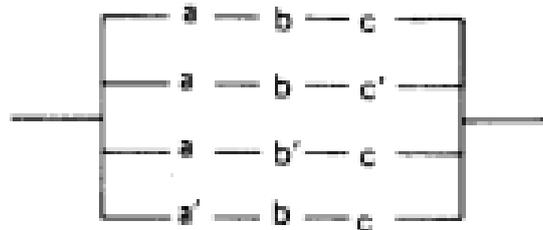

iii)

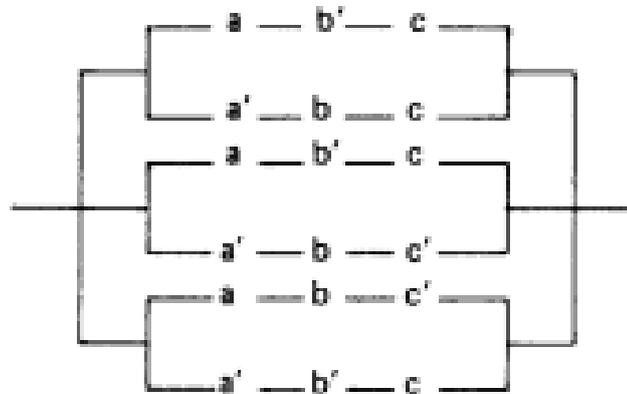

2. Desenhar os circuitos cujas ligações são dadas pelas expressões:

a) $p \cdot (q + r)$

b) $m + (p' \cdot q' \cdot r')$

c) $m + n + p + q$

d) $(x \cdot y) + (x' \cdot z)$

e) $(x' \cdot y) + (x \cdot y')$


f) $(p + q) \cdot (p' + q')$

g) $(p + q) \cdot (p + q' + r')$

h) $(a + b \cdot c) \cdot (a' \cdot b' + c') + a' \cdot b' \cdot c'$

i) $p \cdot [q' \cdot (s + r) + r \cdot s] + (q + p') \cdot (r \cdot s' + s)$

b)

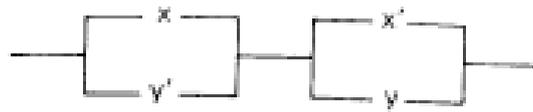

EXERCÍCIOS

1. Dar as expressões algébricas dos circuitos desenhados:

